

EECS150 - Digital Design  
Lecture 23 - Arithmetic and Logic Circuits  
Part 4

April 19, 2005  
John Wawrzynek

Outline

- Shifters / Rotators
  - Fixed shift amount
  - Variable shift amount
- Multiplication Revisited
  - Fixed multiplication value (multiplication by a constant)
  - Variable multiplication value (done last week)


## Fixed Shifters / Rotators

- “fixed” shifters “hardwire” the shift amount into the circuit.

- Ex:  $X \gg 2$   
– (right shift X by 2 places)


- Fixed shift/rotator is nothing but wires!

So what?

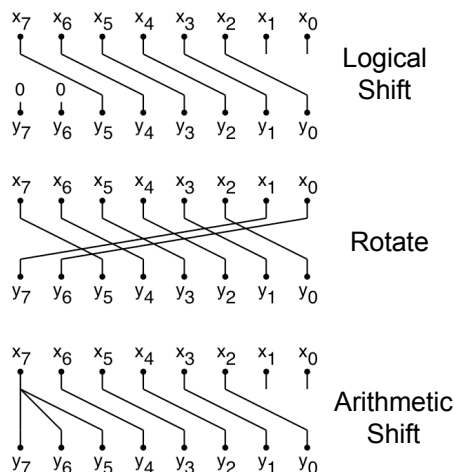

## Variable Shifters / Rotators

 
- Example:  $X \gg S$ , where S is unknown when we design and build the circuit.
- Uses: shift instruction in processors (ARM includes a shift on every instruction), floating-point arithmetic, division/multiplication by powers of 2, etc.
- One way to build this is a simple shift-register:
  - a) Load word,
  - b) shift enable for S cycles,
  - c) read word.



- Worst case delay  $O(N)$ , not good for processor design.
- Can we do it in  $O(\log N)$  time and fit it in one cycle?

## Funnel Shifter / Rotator

- Log(N) stages, each shifts (or not) by a power of 2 places,  $S=[s_2;s_1;s_0]$ :

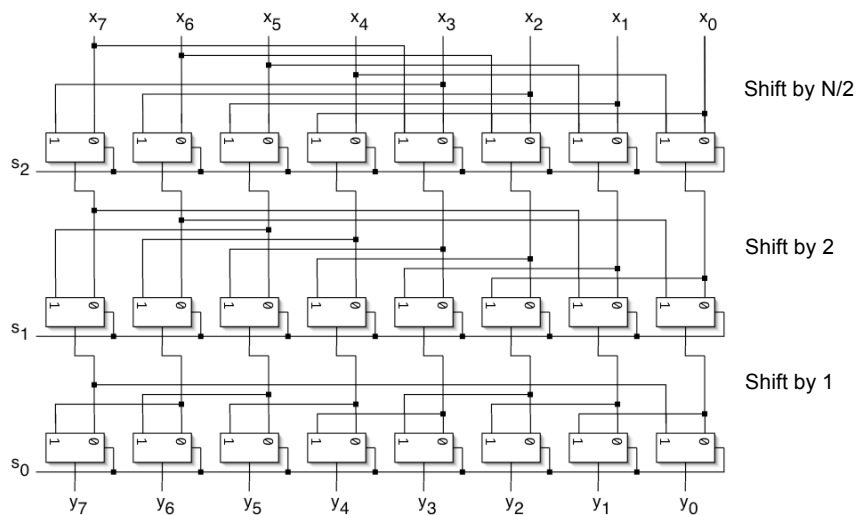


Spring 2005

EECS150 - Lec23-alc4

Page 5
 
## “Improved” Shifter / Rotator

- How about this approach? Could it lead to even less delay?




- What is the delay of these big muxes?
- How about a transistor-level optimization.

Spring 2005

EECS150 - Lec23-alc4


Page 6

## Barrel Shifter

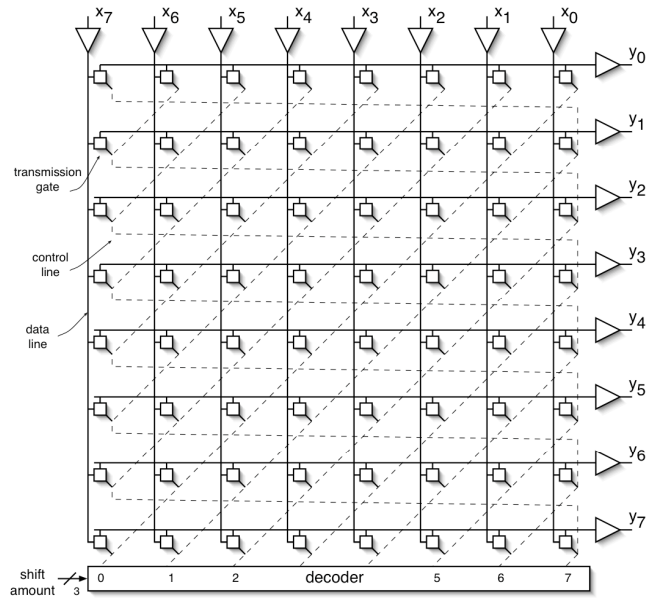

Cost/delay?  
 - (don't forget the decoder)


## Connection Matrix

 

Generally useful structure:

- $N^2$  control points.
- What other interesting functions can it do?

## Cross-bar Switch

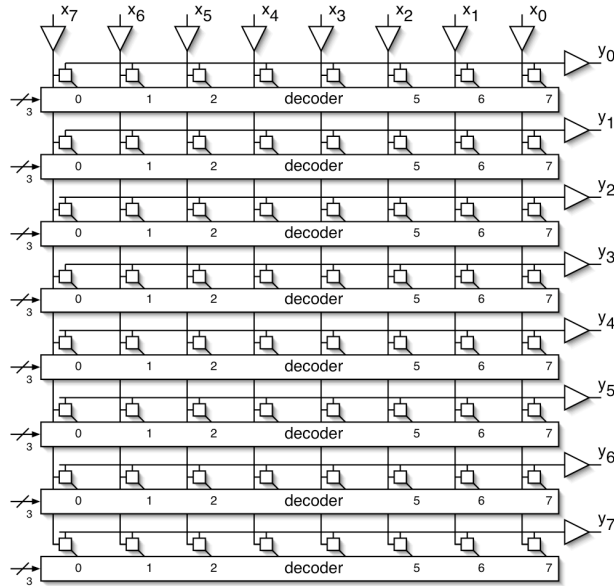

- $N \log(N)$  control signals.
- Supports all interesting permutations
  - All one-to-one and one-to-many connections.
- Commonly used in communication hardware (switches, routers).

Page 9

## Multiplication Revisited

$a_3$	$a_2$	$a_1$	$a_0$	$\leftarrow$	<i>Multiplicand</i>	
$b_3$	$b_2$	$b_1$	$b_0$	$\leftarrow$	<i>Multiplier</i>	
<hr style="width: 50%; margin: 0 auto;"/>						
$X$	$a_3b_0$	$a_2b_0$	$a_1b_0$	$a_0b_0$	}	
	$a_3b_1$	$a_2b_1$	$a_1b_1$	$a_0b_1$		<i>Partial products</i>
	$a_3b_2$	$a_2b_2$	$a_1b_2$	$a_0b_2$		
$a_3b_3$	$a_2b_3$	$a_1b_3$	$a_0b_3$			
<hr style="width: 50%; margin: 0 auto;"/>						
	$\dots$	$a_1b_0 + a_0b_1$	$a_0b_0$	$\leftarrow$	<i>Product</i>	

## Multiplication Revisited

- Our discussion so far has assumed both the multiplicand (A) and the multiplier (B) can vary at runtime.
- What if one of the two is a constant?

$$Y = C * X$$

- “Constant Coefficient” multiplication comes up often in signal processing and other hardware. Ex:


$$y_i = \alpha y_{i-1} + x_i \quad x_i \rightarrow \boxed{\phantom{000}} \rightarrow y_i$$

where  $\alpha$  is an application dependent constant that is hard-wired into the circuit.

- How do we build an array style (combinational) multiplier that takes advantage of the constancy of one of the operands?
 
## Multiplication by a Constant


- If the constant C in  $C*X$  is a power of 2, then the multiplication is simply a shift of X.
- Ex:  $4*X$




- What about division?
- What about multiplication by non-powers of 2?
 
## Multiplication by a Constant

- In general, a combination of fixed shifts and addition:
  - Ex:  $6 \cdot X = 0110 \cdot X = (2^2 + 2^1) \cdot X$



– Details:

 


Spring 2005

EECS150 - Lec23-alc4

Page 13
 
## Multiplication by a Constant

- Another example:  $C = 23_{10} = 010111$



- In general, the number of additions equals one minus the number of 1's in the constant, C.*
- Using carry-save adders (for all but one of these) helps reduce the delay and cost, but the number of adders is still the number of 1's in C minus 1.
- Is there a way to further reduce the number of adders (and thus the cost and delay)?


Spring 2005

EECS150 - Lec23-alc4

Page 14

## Multiplication using Subtraction

- *Subtraction is the same cost and delay as addition.*
- Consider  $C \cdot X$  where  $C$  is the constant value  $15_{10} = 01111$ .
  - $C \cdot X$  requires 3 adders (probably 2 CSA and 1 CPA).
- We can “recode” 15
  - from  $01111 = (2^3 + 2^2 + 2^1 + 2^0)$
  - to  $1000\bar{1} = (2^4 - 2^0)$
  - where  $\bar{1}$  means negative weight.
- Therefore,  $15 \cdot X$  can be implemented with only one subtractor.

 

Spring 2005

EECS150 - Lec23-alc4

Page 15

## Canonic Signed Digit Representation

- CSD represents numbers using 1,  $\bar{1}$ , & 0 with the least possible number of non-zero digits.
  - Strings of 2 or more non-zero digits are replaced.
  - Leads to a unique representation.
- To form CSD representation might take 2 passes:
  - First pass: replace all occurrences of 2 or more 1's:
    - $01..10$  by  $10..\bar{1}0$
  - Second pass: same as above, plus replace  $0\bar{1}10$  by  $00\bar{1}0$
- Examples:

$011101 = 29$	$0010111 = 23$	$0110110 = 54$
$100\bar{1}01 = 32 - 4 + 1$	$001100\bar{1}$	$10\bar{1}10\bar{1}0$
	$010\bar{1}00\bar{1} = 32 - 8 - 1$	$100\bar{1}0\bar{1}0 = 64 - 8 - 2$

- Can we further simplify the multiplier circuits?

Spring 2005


EECS150 - Lec23-alc4

Page 16



 
## “Constant Coefficient Multiplication” (KCM)

Binary multiplier:  $Y = 231 * X = (2^7 + 2^6 + 2^5 + 2^2 + 2^1 + 2^0) * X$




- CSD helps, but the multipliers are limited to shifts followed by adds.

 – CSD multiplier:  $Y = 231 * X = (2^8 - 2^5 + 2^3 - 2^0) * X$



- How about shift/add/shift/add ...?

 – KCM multiplier:  $Y = 231 * X = 7 * 33 * X = (2^3 - 2^0) * (2^5 + 2^0) * X$



- No simple algorithm exists to determine the optimal KCM representation.
- Most use exhaustive search method.